

RAMJAYAM VIDYAA MANDIR MATRIC HR SEC SCHOOL.CUMBUM

Chapter 4to 6

Important 2 Mark 3mark and 5 mark questions & Answers



**D.Easwaran.M.sc B.ed.
Computer instructor.
RJMS –School.**

+1 HIGHER SECONDARY 2MARK 3MARK AND 5 MARK IMPORTANT Q & A

4. WORKING PRINCIPLE OF DIGITAL LOGIC

2 MARK & 3 MARK

1. What is logic circuit?

- ✓ Logic circuit is an elementary building block.
- ✓ It is a circuit with one output and one or more inputs.
- ✓ logic gate takes one of the two binary conditions low (0) or high (1), represented by different voltage levels

12. List the fundamental logical gates?


There are three fundamental logic gates namely, AND, OR and NOT. Also we have other logic gates like NAND, NOR, XOR and XNOR.

3. Why NAND and NOR gates are called as universal gates?

NAND and NOR gates are called the universal gates, because the fundamental logic gates can be realized through them


4. How AND gate can be realized using NOR gate?

a

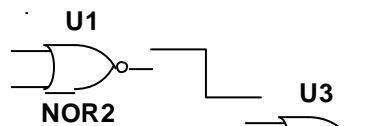

0

b

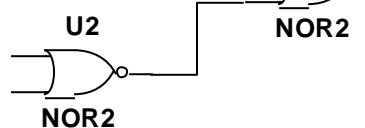


1

$$\begin{aligned} & \overline{\overline{A+B}} \\ & = A+B \\ & \overline{\overline{A+B}} \\ & = A+B \end{aligned}$$

(According to De-Morgan's theorem)

$$=A.B \text{ (AND Gate Output)}$$

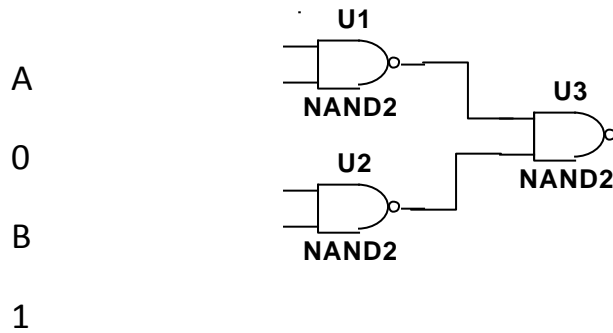
5. How OR gate can be realized using NAND gate?



Here

$$\begin{aligned} &= \overline{\overline{A} \cdot \overline{B}} \\ &= \overline{\overline{A} \cdot \overline{B}} \\ &= A + B \text{ (OR Gate output)} \end{aligned}$$

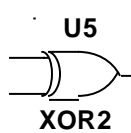6. Give the truth table of XOR gates for two inputs.



$$C = A'B + AB'$$

Input		output
A	B	c
0	0	1
0	1	0
1	0	0
1	1	1

